

CSARCH1 LE2 Reviewer Series


State Reduction

Version: 0.0

Given  $n$  flip-flops, we can have  $2^n$  distinct states. These states can be reduced further by identifying redundant states. After reduction, we can reassign states to certain binary values so that flip-flops can be implemented with minimum number of logic gates.

Example 1:

	Next State		
Present State	$X = 0$	$X = 1$	Output
$A$	$G$	$E$	1
$B$	$H$	$C$	0
$C$	$B$	$D$	1
$D$	$H$	$G$	0
$E$	$H$	$C$	0
$F$	$H$	$I$	0
$G$	$A$	$B$	1
$H$	$G$	$D$	1
$I$	$I$	$E$	1

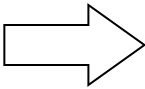

	Next State		
Present State	$X = 0$	$X = 1$	Output
$A$	$G$	$E \rightarrow B$	1
$B$	$H$	$C$	0
$C$	$B$	$D$	1
$D$	$H$	$G$	0
$F$	$H$	$I$	0
$G$	$A$	$B$	1
$H$	$G$	$D$	1
$I$	$I$	$E \rightarrow B$	1

	Next State		
Present State	$X = 0$	$X = 1$	Output
$A$	$G$	$B$	1
$B$	$H$	$C$	0
$C$	$B$	$D$	1
$D$	$H$	$G$	0
$F$	$H$	$I$	0
$G$	$A$	$B$	1
$H$	$G$	$D$	1
$I$	$I$	$B$	1

Two states are equivalent if every possible set of inputs generate the same output and lead to the same next state.